

## Experiment No. 07

**Aim:** - To study and verify Resonance in R-L-C series circuit and measurement of resonance frequency.

**Goal:** -

- Define resonant frequency in series circuit.
- Understand series resonance phenomenon.

**Apparatus:** -

Sr. No.	Apparatus	Range	Qty.
01	Voltmeter		
02	Ammeter		
03	Resistance		
04	Chock coil		
05	Capacitor		
06	A.C. Supply		
07	Connecting wires		

**Theory:-**

Consider an AC-series circuit in which the resistance, inductance and capacitor are connected in series across a variable frequency A.C. source.

Let, impedance of the circuit,

$$Z = R + j(X_L - X_C)$$

Now, if the frequency is increased  $X_L$  increase and  $X_C$  decrease. Resistance is not dependent on Frequency of source.  $X_L$  can be made equal to  $X_C$  at one frequency.

$$|Z| = \sqrt{R^2 + (X_L - X_C)^2}$$

Where,  $X_L = 2\pi fL$  and  $X_C = \frac{1}{2\pi fC}$

Such a circuit shown in figure 1 is connected to an A.C source of constant supply voltage V but having variable frequency. The frequency can be varied from zero, increasing and approaching infinity. Since  $X_L$  and  $X_C$  are functions of frequency at a particular frequency of applied voltage  $X_L$  and  $X_C$  will be become equal in magnitude.

$$\text{Since, } X_L = X_C$$

$$X_L - X_C = 0$$

$$\text{So, } Z = \sqrt{R^2 + 0}, Z=R.$$

The circuit, when  $X_L = X_C$  & hence  $Z = R$  is said to be in resonance in a series circuit since current  $I$  remains same.

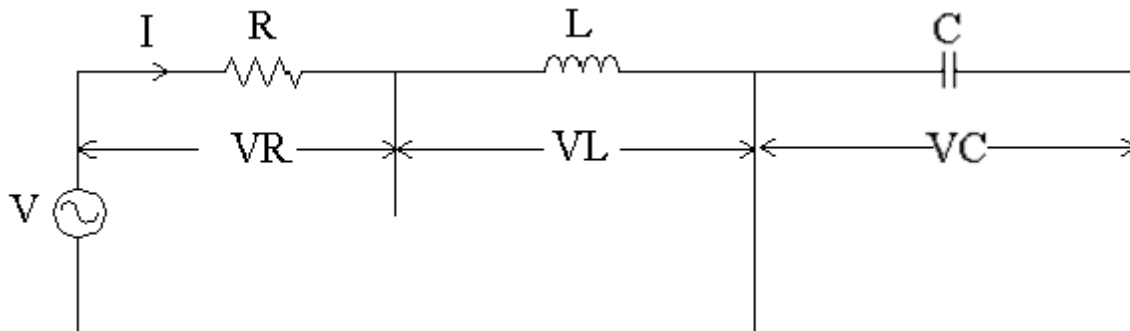


Figure 1

$$IX_L = IX_C$$

$$V_L = V_C$$

So at resonant  $V_L$  and  $V_C$  will be canceling out each other.

$$\text{The supply voltage, } V = \sqrt{V_R^2 + (V_L - V_C)^2}$$

$$V = \sqrt{V_R^2}$$

$$V = V_R$$

The phasor diagram is shown in figure 2.

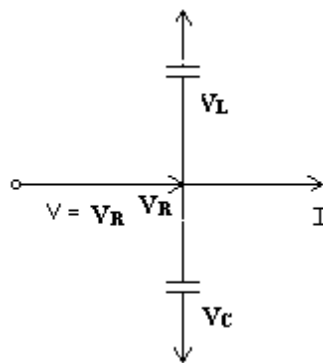


Figure 2

The phasor diagram shown in figure can be redrawn as shown in figure 3.

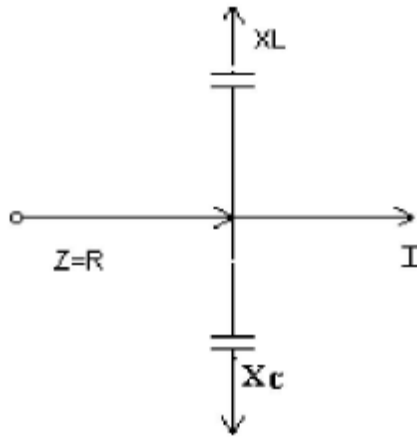


Figure 3

This is equal to supply voltage and current in phase as shown in figure 4.

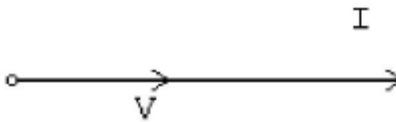


Figure 4

Now, Resonant frequency [At resonant condition  $X_L = X_C$ ]

$$2\pi f_r L = \frac{1}{2\pi f_r C}$$

$$f_r^2 = \frac{1}{4\pi^2 LC}$$

$$f_r = \frac{1}{2\pi\sqrt{LC}}$$

L=inductance in Henry

C=capacitance in farads

$f_r$  = resonant frequency in HZ

#### EFFECT OF SERIES RESONANCE: -

1. When a series R-L-C circuit at resonance  $X_L = X_C$ , the net reactance of circuit is zero.
2.  $Z = R$ , then the impedance of circuit is minimum.

3.  $I = V/Z$  Here  $Z$  is minimum, so  $I$  is maximum.
4. Since,  $I$  is maximum, the power dissipated would be maximum  $P = I^2R$ .
5.  $V_L = V_C$ ,  $V = V_R$  i.e. since supply voltage is in phase with the supply current  $I$ . Hence power factor angle  $\Phi = 0$ . And circuit power factor  $\cos\Phi = \cos 0 = 1$

**Circuit Diagram:-**

**Procedure: -**

- Connect the circuit as per circuit diagram.
- Set suitable value of the parameter from decade box and switch on the supply. Adjust minimum frequency of the supply.
- Increase the frequency gradually and note down the current flowing through the circuit.
- Continue to increase the frequency and not down the reading until the current increases to maximum and starts decreasing.
- Plot the graph of current v/s frequency.
- Obtain the resonance frequency from graph and also calculate resonance frequency from equation.

**Observation Table:-**

<b>Sr. No.</b>	<b>Frequency in Hz</b>	<b>Current mA</b>
01		
02		
03		
04		
05		
06		
07		
08		
09		
10		
11		
12		
13		
14		
15		

**Calculations:-**

**Conclusion:-**